

# ELECTRICAL MACHINES

## ELECTRICAL ENGINEERING

# Theory & Objective

*By  
Team of  
Engineers Academy*

- Covers ESE, GATE, IAS, State PCS, BSNL(JTO) DRDO, ISRO, and Other PSUs Exams.
- Covers all topics of GATE & ESE objective papers.
- Covers complete syllabus of GATE & ESE examination.
- Highlights all topics.



# ENGINEERS ACADEMY™

**Your GATEway to Professional Excellence**

**IES • GATE • PSUs • JTO • IAS • NET**

**Corporate Office :** 100-102, Ram Nagar, Bambala Puliya, Pratap Nagar, Jaipur-302033

**Ph.:** 0141-6540911, +91-8094441777

**Website :** [www.engineersacademy.org](http://www.engineersacademy.org) | **Email:** [info@engineersacademy.org](mailto:info@engineersacademy.org)

Ajmer | Jaipur | Kota | Jodhpur | Bhilwara | Delhi | Patna | Lucknow | LPU | Ludhiana | Jalandhar | Kanpur

# ESE GATE

JEn  
JTO  
TTA

# PSU

अतुल्य | EA

*Again we proved  
"We are history maker"*

GATE-2016

**2**  
AIR



**AVINASH SHAH**  
EA Roll No. : IN102/2015-16

**2**  
AIR



**ABHAMANU JAIN**  
RPSC : AEn



**Ramavtar Meena**  
Roll No. : 13NBC15106129  
Branch : Civil, NBCC  
Post : Junior Engineer

## GATE-2016 : TOPPERS



Rukhsar AIR-7 (EE)	Ashish Tripathi AIR-15 (PI)	Prateek AIR-28(ME)	Arman Kataria AIR-39 (IN)	Bhanuday AIR-56(EE)	Ashok Kr. Jat AIR-62 (CE)	Rajat Sharma AIR-75 (ME)	Rachit Kumar AIR-90(EE)	Amit Kumar AIR-92 (ME)
Nitin AIR-145 (EE)	Shivam Sharma AIR-303(EE)	Rahul Gupta AIR-334 (CE)	Kshij Kansal AIR-336 (ME)	Leeladhar AIR-342 (EIC)	Purav AIR-378(ME)	Ram Singh AIR-382 (CE)	Mahesh Kumar AIR-394 (CE)	Krishnakant AIR-410 (CE)

many results are awaited...

## ESE TOPPERS



Deepika Gill AIR-5 (CE)	Kirti Kaushik AIR-7 (CE)	Pawan AIR-22 (EE)
Ran Singh AIR-22 (ECE)	Sanapala AIR-22 (CE)	Yogesh AIR-33 (EE)
Ajit Kumar AIR-37 (EC)	Abhishek AIR-37 (ME)	Aditya Amber AIR-46 (EC)
Mohan AIR-50 (EE)	Devi Shankar AIR-57 (ME)	Kishan AIR-63 (ME)

## JTO & TTA TOPPERS



Tajpal Kasana	Mahesh Khayani	Anurag Sharma
Bhagirath Meena	Babudi	Kamlesh Meena
Sanjay Singh	Naresh Sahoo	Pradeep Palwal
Rajnish Meena	Arun Kumar	Mukul Palwal

## AEn & JEn TOPPERS



Arun Sharma	Prashant Palwal	Samsad
Rahul	Santosh Kanwar	Yogesh Kumar
Meenu Kanwar	Sunil Kumar	Amita Bhaskar
Prakash Kumar	Ruchika Tak	Raj Singh

स्वायत्त शासन विभाग राज. सरकार (राजस्थान नगर पालिका)

## सहायक अभियंता



<b>Rank 8</b> Chirag Goyal Roll No. : 21414346670 Civil : Assistant Engineer	<b>Rank 39</b> Rahul Kumar Bhatta Roll No. : 22046373468 Civil : Assistant Engineer	<b>Rank 45</b> Pralibha Kuri Roll No. : 11630363603 Civil : Assistant Engineer	<b>Rank 46</b> Sukhpal Kaur Roll No. : 31452341723 Civil : Assistant Engineer
---	--	---	--

## WRD : 2016 Selection



Anil Bishnoi CE: WRD-JEn	Dharmendra Singh CE: WRD-JEn	Rohit Gurjar CE: WRD-JEn	Jaidev Solanki CE: WRD-JEn	Ramavtar Lamba CE: WRD-JEn	Manish Kumar CE: WRD-JEn
Pooja Sharma CE: WRD-JEn	Sumit Mahar CE: WRD-JEn	Avinash CE: WRD-JEn	Ankush Jain CE: WRD-JEn	Poonam Chand CE: WRD-JEn	



# ENGINEERS ACADEMY

Your GATEway to Professional Excellence

IES • GATE • PSUs • JTO • IAS • NET

Ph. : 0141-6540910 / 111, +91-8094441777 / 999

Website : [www.engineersacademy.org](http://www.engineersacademy.org) | Email: [info@engineersacademy.org](mailto:info@engineersacademy.org)

Ajmer | Jaipur | Kota | Jodhpur | Bhilwara | Delhi | Patna | Lucknow | LPU | Ludhiana | Jalandhar | Kanpur

# CONTENTS

S.No.	Topic	Page No.
1.	Transformers .....	1 – 60
	Objective Sheet.....	61 – 79
2.	Electromechanical Energy Conversion Principles .....	80 – 89
3.	DC Machines.....	90 – 146
	Objective Sheet.....	147 – 151
4.	Induction Motors .....	152 – 218
	Objective Sheet.....	219 – 222
5.	Three Phase Synchronous Machines .....	223 – 281
	Objective Sheet.....	282 – 287
6.	Stepper & Servo Motor.....	288 – 293
	Objective Sheet.....	294 – 296



**ENGINEERS ACADEMY**  
**PUBLICATIONS**

Log on to : [www.eapublications.org](http://www.eapublications.org) | Ph. : 08094441777

Visit us:  
www.engineersacademy.org

WhatsApp :  
+91-8094441777

engineersacademyindia.blogspot.in



Facebook :  
Engineersacademy.org

SMS :  
+91-8094441999

AcademymyIndia

# Institute for ESE • GATE • PSUs • JEn

## ESE : TOPPER



Deepika Gill  
AIR-5 (CE)



Atesh Kumar  
AIR-12 : EC



Sushant Parashar  
AIR-16 (EE)



Naveen Joshi  
AIR-17 : EC



Rohit Mahes.  
AIR-19 : CE



Pawan  
AIR 22 (EE)



Ran Singh  
AIR - 22 (ECE)



Sanapala Abhiram  
AIR-23 (CE)



Sandeep Dhaked  
AIR-31(ECE)



Saurabh  
AIR-31 : ME



Yoges  
AIR-33 : EE



Abhishek  
AIR-37 (ME)



Neelanshee  
AIR-38 : EE



Sheetanshu Tiwari  
AIR-47 (EE)



Aditya Amber  
AIR-46 : EC



Gaurav Jasuja  
AIR-52 : EE



Neha Mehta  
AIR-53 : CE



Saurabh Singh  
AIR-56 : CE



Devi Shankar  
AIR-57 : ME



Krishan  
AIR-63 (ME)



Pramod Dudi  
AIR-67 : ME



Prashank  
AIR-69 (EE)



Neelu Sreekumar  
AIR-72 (ECE)



Narain Pratap  
AIR-73 : CE



Ravi Kumar  
AIR-76 : CE



Anuj Kushari  
AIR-78 : CE



Upkar Pathak  
AIR-81 (CE)



Shri Krishan  
AIR-87 : ME



Sandeep  
AIR-94 : EC



Rampukar Raman  
AIR-94 : ME



Prince Bhati  
AIR-111 : ME



Bhaskar  
AIR-120 : ME



Kalindi  
AIR-122 : ME



Meer Singh  
AIR-127 : EE



## PSUs : TOPPER



Raj Kumar (Branch : EE)  
SSC-JEn, RRB-SSE  
1st Rank: Odonil Factory



Himanshu Bhaskar  
Branch : CE  
NITIE-Bombay



Shreyansh Dhanekar  
Branch : CS & IT  
IISc, Bangalore



Ranjeet Kumar Gupta  
Branch : ME  
IOCL



Prakash Kumawat  
Branch : EE  
BEL



Shyam Sundar Pareek  
Branch : EE  
BEL



Vishal Sharma  
Branch : ME  
JINDAL SAW Ltd.



Ankit Gupta  
Branch : EE  
HPCL, THDC



Dharmanshu Mittal  
Branch : ME  
BARC



Pavan Kumar Nagar  
Branch : CE  
BARC



Swarupa  
HPCL



Alok Kumar  
Branch : EE (HAL)



Ajeet Vagle  
Branch : EE(NTPC)



Prachi Adity  
BHEL



Paras Bareja  
Branch : EE(IOCL)



Smita Gupta  
Branch : AAI



Ratan Kumar  
NTPC



Kuldeep  
BSNL-JTO

Admission Open for ESE, GATE, PSUs, JEn, JTO, TTA & Other Technical Competitive Exam



**ENGINEERS ACADEMY**  
Your GATEway to Professional Excellence  
IES • GATE • PSUs • JTO • IAS • NET

### Corporate Office :

100-102, Ram Nagar, Bambala Puliya,  
Pratap Nagar, Jaipur  
Ph.: 0141-6540911

### Head Office :

40-Kailashpuri, Near Khandaka Hospital,  
Gopalpura, Tonk Road, Jaipur  
Ph.: 0141-6540910

Every Thing in This World is Directly or Indirectly Related to Engineering

<b>DELHI</b> (+91-7239992777)	<b>KANPUR</b> (+91-7239992111)	<b>AJMER</b> (+91-7737278888)	<b>BHILWARA</b> (+91-9351770644)	<b>JALANDHAR</b> (+91-7589441777)	<b>JAIPUR</b> (+91-8094441999)	<b>JODHPUR</b> (+91-9928665551)
<b>KOTA</b> (+91-8290256342)	<b>LPU CAMPUS</b> (+91-9465220033)	<b>LUDHIANA</b> (+91-9888928477)	<b>LUCKNOW</b> (+91-7080555455)	<b>PATNA</b> (+91-8434441777)	<b>SIKAR</b> (+91-8094401333)	



# TRANSFORMERS

## THEORY

A Transformer is a static device comprising coupled coils (Primary and Secondary) wound on common magnetic Core.

MMF (F)

$$F = NI \text{ Amp. turns}$$


Let the mean core length =  $l$

Flux density = B, Flux  $\phi = BA$

A = Area of cross-section of core.


Magnetization force or magnetic field intensity (H)
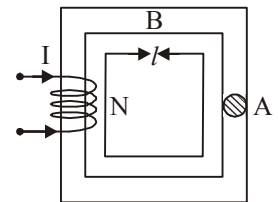
$$H = \frac{NI}{l} \text{ AT}^s / \text{m}$$


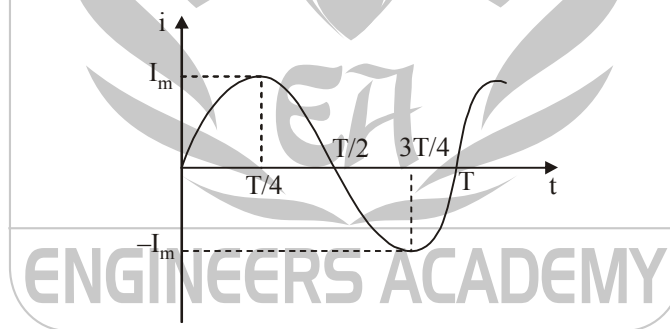
### 1.1 MAGNETIC HYSTERESIS CURVE

If ac current is made to flow through coil in the magnetic circuit shown above  $i = I_m \sin \omega t$



Time period  $T = \frac{1}{f} = \frac{2\pi}{\omega}$

Where  $\omega = 2\pi f$  is frequency

Let initially  $B = 0$  (i.e. residual magnetism is absent)

For  $0 < t < \frac{T}{4}$  where  $i$  increases from zero to  $I_m$  initially B increases linearly with H (or  $i$ ) and after a certain value of H, B doesn't increase significantly i.e. B remains almost constant i.e. saturation.





For linear magnetic circuit

$$B \propto H$$

$$\Rightarrow B = \mu H$$

$$\Rightarrow B = \mu_0 \mu_r H$$

Where  $\mu$  = Permeability of iron core


$\mu_r$  = Relative permeability of core

$\mu_0$  = Permeability of air

Flux linking  $\phi = BA = \mu HA = \mu A \times \frac{Ni}{l} \quad (H = \frac{Ni}{l})$

$$\Rightarrow \phi = \frac{Ni}{l} = \frac{F}{Rl}$$

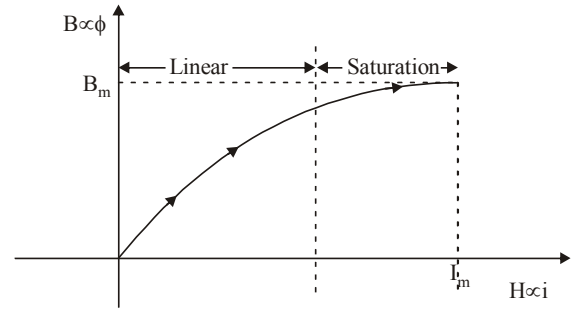Where  $F = Ni$  (mmf in Amp-Turns) applied



$$R_l = \frac{l}{\mu A} \text{ reluctance of core}$$

mmf = Magneto-Motive Force

The equation  $\phi = \frac{F}{R_l}$  is developed on basis of the analogy of electrical circuit (force voltage analogy)

shown below :


$$\text{Current} = \frac{\text{EMF}}{\text{Resistance}}$$

$$\Rightarrow i = \frac{e}{R}$$

Where resistance

$$R = \frac{l}{\sigma A} \quad \left( R = \frac{1}{G} = \frac{1}{\sigma A / l} = \frac{l}{\sigma A} \right)$$

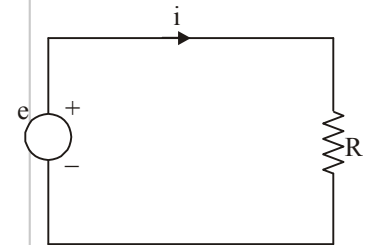$l$  &  $A$  are the length & area of cross-section while  $\sigma$  is the conductivity of material.



$$\text{Flux} = \frac{\text{mmf}}{\text{Reluctance}}$$

$$\Rightarrow \phi = \frac{F}{R_l}$$

**Note :** For high permeability material e.g. Iron,  $\mu_r$  is high &  $R_l$  is low it is said to be magnetic conductor or magnetic material. For low permeability material  $\mu_r \approx 1$  e.g. Cu etc.  $R_l$  is high so it is said to be non-magnetic material or magnetic insulator.

After  $\frac{T}{4}$  i.e.  $\frac{T}{4} < t < \frac{T}{2}$  where  $i$  decreases from  $I_m$ ,  $B$  also decreases but not in the same manner.






At

$$t = \frac{T}{2}, i = 0 \text{ but } B = B_r \neq 0 \text{ i.e. some residual magnetism is left.}$$

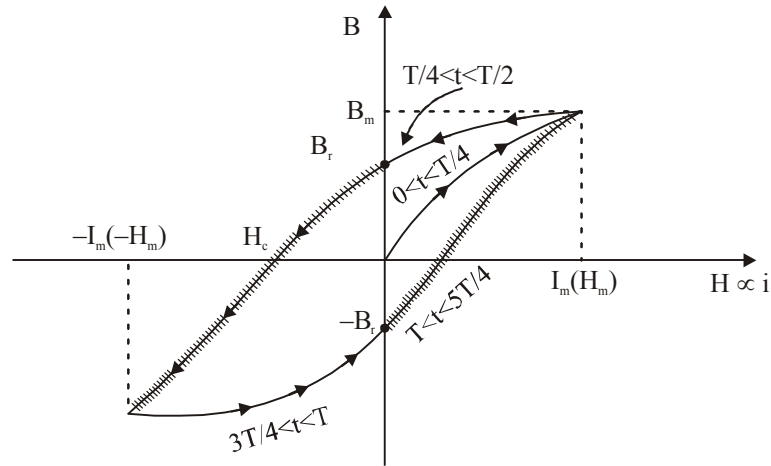$B_r$  = Retentivity or Residual flux density.



After  $\frac{T}{2}$  i.e.  $\frac{T}{2} < t < \frac{3T}{4}$  the direction of current  $i$  (&  $H$ ) gets reversed so magnetization is going on decreasing

and at a particular value of current say  $I_c$  (&  $H_c = \frac{NI_c}{l}$ )  $B$  becomes zero i.e. residual magnetism is lost due to  $H_c$ .

$H_c$  = Coercivity or Coercive force

As  $i$  increases further (in -ve direction)  $B$  gets reversed & becomes max at  $t = \frac{3T}{4}$ .

⇒

$$P_h \propto B_m^x f$$


$$P_h = K_h B_m^x f$$

Where  $x$  = Steinmetz constant ( $x = 1.6$ ),  $K_h$  = Hysteresis coefficient

According to B-H loop we categorize magnetic material broadly into two categories

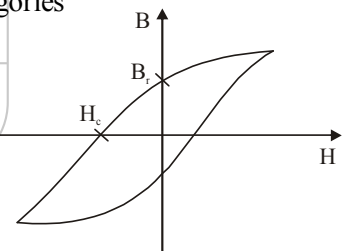
### Hard Magnetic Material

- Wider B-H loop
- $B_r, H_c$  (Both high)
- Hysteresis loss Higher
- Suitable for d.c applications & permanent magnet etc.


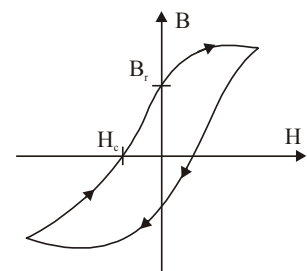
### Soft Magnetic Material

- Narrow B-H loop
- $B_r, H_c$  (both low)
- Hysteresis loss small
- Used for a.c applications e.g. Transformer, AC machines.





Let us neglect hysteresis & saturation, the B-H loop will be linear (as in case of air)

According to B-H loop

$$B \propto H$$


$$B = \mu H$$

$\mu$  = Permeability of core

$$\mu = \mu_0 \mu_r$$

$\mu_0$  = Absolute Permeability

$\mu_r$  = Relative Permeability

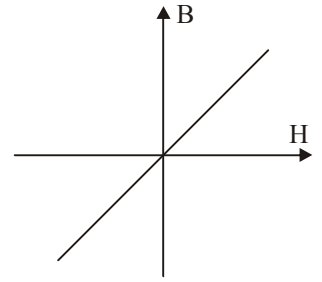


For linear magnetic circuit

$$\phi \propto I$$

$$\phi = \frac{\text{mmf}}{\text{Reluctance}} = \frac{F}{R_l}$$
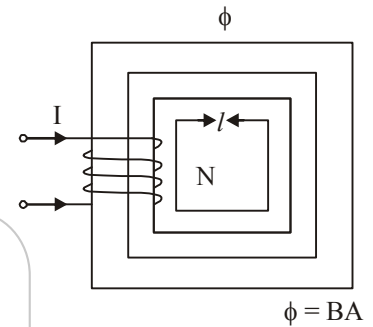
$$\phi = BA \left( \because B = \frac{\mu NI}{l} \right)$$



$$\phi = \frac{\mu NI}{l} \cdot A$$

$$\phi = \frac{NI}{(l/\mu A)} = \frac{\text{mmf}}{\text{Reluctance}}$$

$$\text{Reluctance} = \frac{l}{\mu A}$$

$$\phi = \frac{\mu NIA}{l}$$

Flux linkage

$$\psi = N\phi$$

$$N\phi \propto I$$

$$N\phi = LI$$

Inductance

$$L = \frac{N\phi}{I} \text{ i.e. flux linkage per unit current.}$$

$$L = \frac{N\phi}{I} = \frac{N}{I} \left( \frac{\mu NIA}{l} \right)$$

$$L = \frac{\mu N^2 A}{l}$$

⇒

$$L = \frac{N^2}{(l/\mu A)} = \frac{N^2}{R_l}$$







$R_l = \text{Reluctance}$

$\therefore$

$$L \propto \frac{1}{R_l}$$

Air gap length =  $l_g$

$R_l = \text{Reluctance of iron path}$

$R_g = \text{Reluctance of air path}$

Total Reluctance in the path of flux,  $\phi$

$$R_l = R_l + R_g$$

For iron path

$$R_l = \frac{l_i}{\mu_0 \mu_r A}$$

$\mu_r \rightarrow \text{Relative Permeability of iron.}$

For airgap,

$$R_g = \frac{l_g}{\mu_0 A}, \text{ As } (\mu_r = 1) \text{ for air}$$

As Permeability of iron is much greater than permeability of air ( $\mu_r = 1$ )

i.e


$$\mu_r \gg 1$$

So, there fore we can say Reluctance of air gap will be more.

i.e.


$$R_g \gg R_l$$

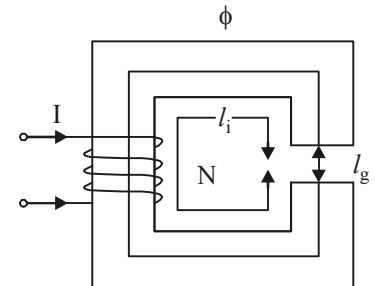i.e. Total reluctance  $R_l \approx R_g$  (air gap reluctance).



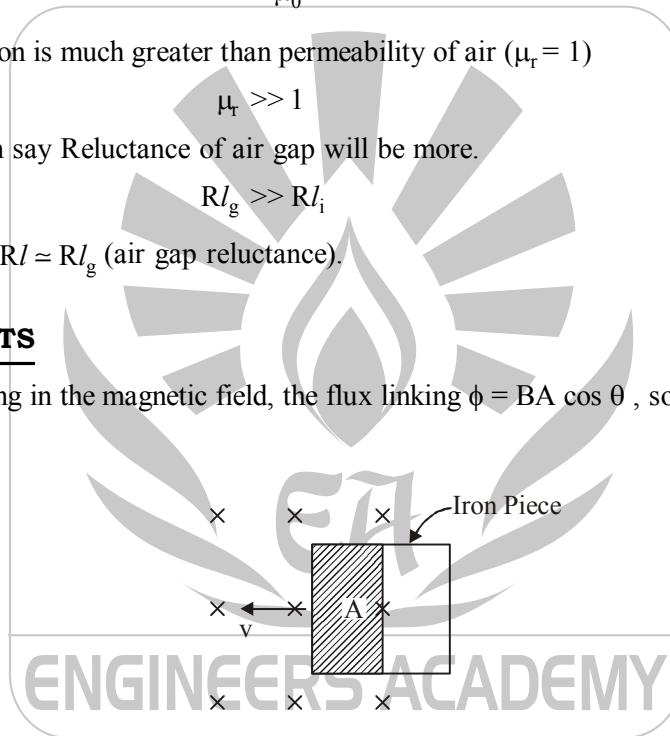
## 1.2 EDDY CURRENTS

If an iron piece is lying in the magnetic field, the flux linking  $\phi = BA \cos \theta$ , so  $\phi$  can be changed if either B, A or  $\theta$  changes.



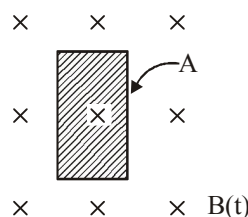**Case-I :** B is constant but area 'A' of iron piece linking with B is changing (e.g. in dc machines) i.e.  $\phi = BA$  also changing with time.





**Case-II :** Iron piece is stationary but B is changing w.r.t time (e.g. transformers), so  $\phi = BA$  is changing w.r.t time.

As flux linking  $\phi(t)$  is changing (in both the cases) there is induced emf in the iron piece i.e.

$$e \propto - \frac{d\phi}{dt}$$


Due to the induced emfs, there are induced currents in the iron i.e. eddy currents  $i_e$

$$i_e = \frac{e}{R_e}$$

Where  $R_e$  is the resistance in the path of eddy currents i.e. resistance of iron.

Eddy current loss i.e. power loss due to eddy currents

$$P_e = i_e^2 R_e = \frac{e^2}{R_e}$$

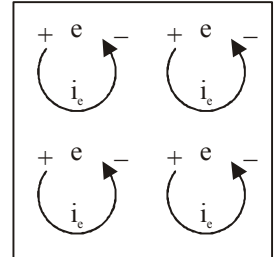


As 'e' is independent of  $R_e$

$$\Rightarrow P_e \propto \frac{1}{R_e}$$

So  $P_e$  can be reduced by increasing  $R_e$  i.e. using high resistivity iron.

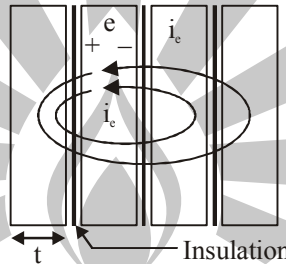
$R_e$  can also be increased if instead of thick iron, laminated iron is used i.e. thin layers of iron pieces are separated by very thin layers of insulation.



As resistance is introduced in the path of eddy currents so resistance  $R_e$  increases & hence power loss decreases.

Where 't' is thickness of lamination.

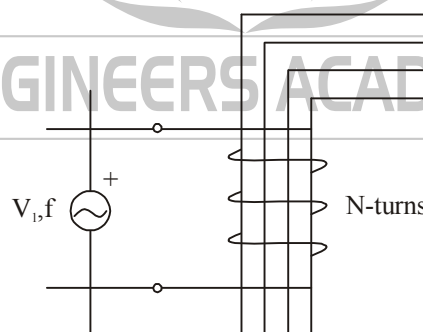Consider the laminated iron core of transformer



The eddy current losses are

$$P_e \propto \frac{\pi^2 B_m^2 f^2 t^2}{\rho_e \beta}$$



Where  $B_m$  is peak flux density in the core

$f$  is frequency

$t$  is thickness of lamination

$\rho_e$  is resistivity of iron core

$\beta$  is constant (depending upon the shape & size of lamination).

$P_e$  can also be reduced by using high resistance of iron core.

$$P_e \propto B_m^2 f^2 t^2$$

or

$$P_e \propto B_m^2 f^2$$

$\Rightarrow$

$$P_e = K_e B_m^2 f^2$$

Where  $K_e$  is constant

The combination of hysteresis loss  $P_h$  & eddy current loss  $P_e$  is said to be iron loss.

$$P_i = P_h + P_e = K_h B_m^{1.6} f + K_e B_m^2 f^2$$

### 1.3 TRANSFORMER EQUATION

**Primary :** Where source is connected.

**Secondary :** Where load is connected.

**At No load.** Due to magnetising current  $I_m$  magnetising flux  $\phi_m$  is produced.

Let  $\phi_m = \phi_{\max} \sin \omega t$

Induced emf in Primary and secondary is  $e_1$  &  $e_2$

$$e_1 = -\frac{N_1 d\phi_m}{dt}, e_2 = -\frac{N_2 d\phi_m}{dt}$$

$$e_1 = -N_1 \frac{d}{dt} (\phi_{\max} \sin \omega t)$$

$$e_1 = -N_1 \omega \phi_{\max} \cos \omega t$$

$$e_1 = -N_1 \omega \phi_{\max} \sin(90 - \omega t),$$

As

$$e_1 = N_1 \omega \phi_{\max} \sin(\omega t - 90^\circ)$$

peak emf

$$E_m = N_1 \omega \phi_{\max}$$

We can say induced emf  $\bar{E}$  lags behind the corresponding flux  $\phi_m$  by  $90^\circ$

$$e_i = N_1 \omega \phi_{\max} \sin(\omega t - 90^\circ)$$

$$e_i = E_m \sin(\omega t - 90^\circ)$$


Peak emf

$$E_m = N_1 \omega \phi_{\max}$$

$$= N_1 (2\pi f) \phi_{\max} = 2\pi f N_1 \phi_{\max}$$

Let r.m.s value of  $E_m$  is  $E_1$
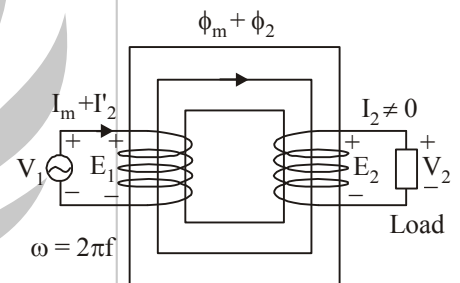
$$E_1 = \frac{E_m}{\sqrt{2}} = \sqrt{2} \pi f N_1 \phi_{\max}$$



ENGINEERS ACADEMY



Similarly

$$E_2 = \sqrt{2}\pi N_2 f \phi_{\max}$$

$$\frac{E_2}{E_1} = \frac{N_2}{N_1}$$

$$\frac{N_2}{N_1} = K$$

Turns ratio or Transformation ratio

As

$$V_1 \approx E_1$$

$$V_1 \approx \sqrt{2}\pi f N_1 \phi_{\max}$$

$$\phi_{\max} = \frac{1}{\sqrt{2}\pi N_1} \frac{V_1}{f}$$

$$\phi_{\max} = \frac{1}{\sqrt{2}\pi N_1} \left( \frac{V_1}{f} \right)$$

$$\phi_{\max} \propto \frac{V_1}{f}$$

$$\phi_{\max} = \text{constant}$$

$$\phi_m = \frac{N_1 I_m}{R_l} \text{ \& Secondary flux } \phi_2 = \frac{N_2 I_2}{R_l}$$

According to Lenz's law the flux  $\phi_2$  of current  $I_2$  will oppose  $\phi_m$ .

**Lenz's law :** The induced current flows in such a direction so as to oppose very cause of its production.

So net flux in core =  $\phi_m - \phi_2$

Due to flux  $\phi_2$  net flux in the core decreased,  $(\phi_m - \phi_2)$

However

$$\phi_m \propto \frac{V_1}{f} = \text{constant,}$$

That's why to maintain flux  $\phi_m$  constant the primary winding produces additional flux  $\phi_2$ , so it takes additional current  $I_2'$

Secondary flux

$$\phi_2 = \frac{N_2 I_2}{R_l}$$

Additional flux by Primary

$$\phi_2 = \frac{N_1 I_2'}{R_l}$$

∴

$$\phi_2 = \frac{N_1 I_2'}{R_l} = \frac{N_1 I_2}{R_l}$$

$$N_1 I_2' = N_2 I_2$$



Primary Current  $\bar{I}_1 = \bar{I}_m + \bar{I}'_2$

As  $\bar{I}_m \ll \bar{I}'_2$

$$I_1 \approx I_2$$

so  $N_1 I_1 \approx N_2 I_2$

This equation is valid only when magnetising current is negligible.

**Example 1**

**Note :**  $E_1 \approx V_1$



$$V_1 = \bar{E}_m + \bar{I}_m (R_1 + jX_1)$$

**Solution**

Let  $\bar{I}_1$  at lag pf  $\cos \phi$

$\bar{I}_1$  lags  $\bar{E}_1$  by angle  $\phi$

At lagging

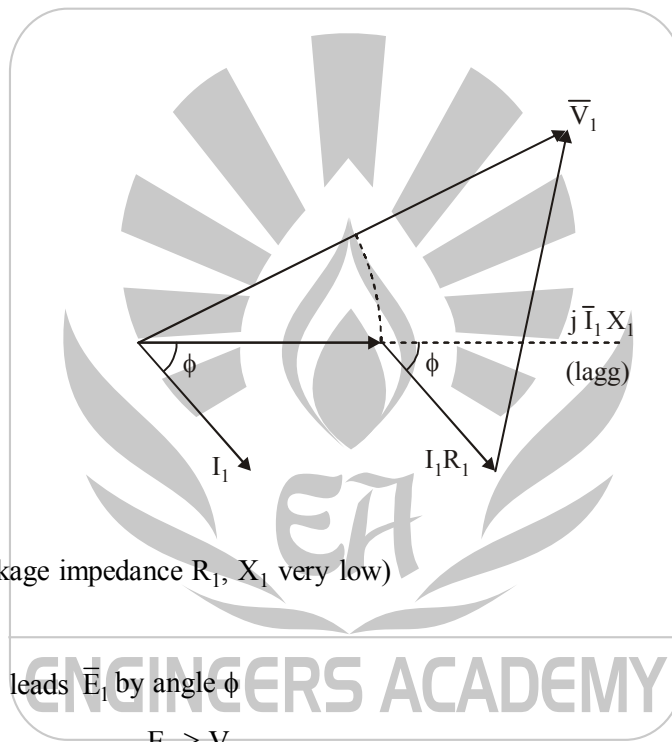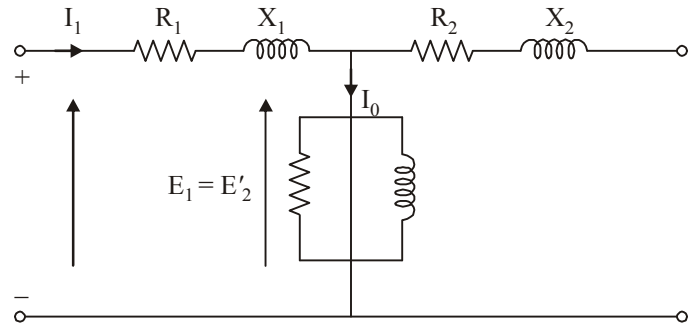


So  $E_1 \leq V_1$  (As leakage impedance  $R_1, X_1$  very low)

At leading pf  $\cos \phi$

$\bar{I}_1$  leads  $\bar{E}_1$  by angle  $\phi$

$$E_1 \geq V_1$$

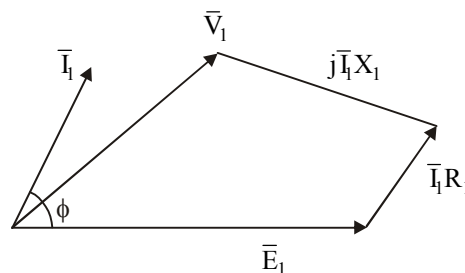



**Example 2 :** The useful flux of a Transformer is 1Wb. when it is loaded at 0.8pf lag, then its mutual flux

- (a) May decrease to 0.8Wb
- (b) May increase to 1.01Wb
- (c) Remains constant
- (d) May decrease to 0.99Wb

**Ans.(d)**

**Solution:** At no load ( $I = 0$ )

$$V_1 \approx E_1$$

$$E_1 = \sqrt{2}\pi f N_1 \phi_m$$

$$\phi_m = \frac{1}{\sqrt{2}\pi N_1} \frac{E_1}{f}$$

At no load

$$E_1 \approx V_1$$


$$\phi_{mo} = \frac{1}{\sqrt{2}N_1\pi} \left( \frac{V_1}{f} \right) = 1\text{Wb}$$

At lag pf  $E_1$  decreases slightly ie  $E_1 \leq V_1$

So 
$$\phi'_m = \frac{1}{\sqrt{2}\pi N_1} \left( \frac{E_1}{f} \right) \leq \phi_{mo}$$

So magnetising flux decreases slightly ie approx 0.99 Wb

### Equivalent Circuit of Transformer

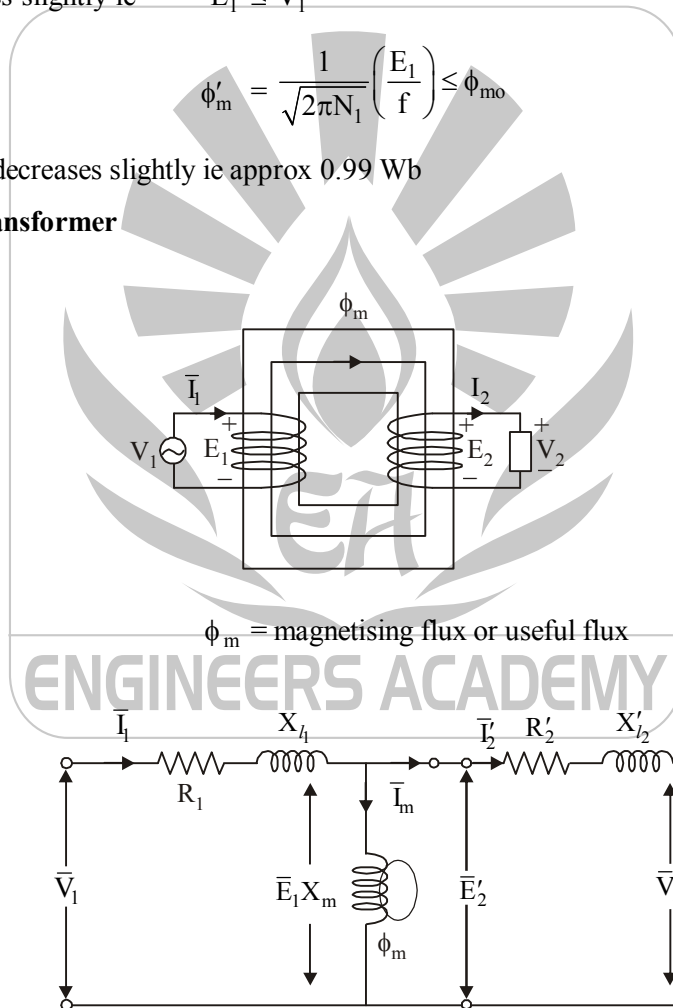

$R_1 =$  Resistance of Primary





$R_2$  = Resistance of Secondary

$X_{l1}$  = Leakage Reactance of Primary

$X_{l2}$  = Leakage Reactance of Secondary

$X_m$  = Magnetising Reactance

Leakage flux through air =  $\phi_l$

$\therefore \phi_m \gg \phi_l$

Total flux  $\phi = \phi_m + \phi_l$

$L = L_m + L_l$

(because  $N\phi = LI$ )

$\phi \propto L$

Where  $L_m$  = Magnetising inductance

$L_l$  = Leakage inductance

$L = L_m + L_l$

Multiplying both side by  $\omega$

$\omega L = \omega L_m + \omega L_l$

$X = X_m + X_l$

$X_m$  = Leakage Reactance

$X_l$  = Magnetising Reactance

Magnitude of e

$$e = \underbrace{N \frac{d\phi}{dt}}_{\text{induced emf}} = \underbrace{L \frac{di}{dt}}_{\text{voltage drop across L}}$$

From the equivalent circuit we can write

$$E_2 = V_2 + I_2 (R_2 + jX_{l2})$$

$$\frac{E_2}{K} = \frac{V_2}{K} + (KI_2) \left( \frac{R_2}{K^2} + j \frac{X_{l2}}{K^2} \right)$$

$$E'_2 = V'_2 + I'_2 (R'_2 + jX'_{l2})$$

Compare above equations :

$$E'_2 = \frac{E_2}{K} = \text{Secondary emf referred to Primary}$$

$$V'_2 = \frac{V_2}{K} = \text{Secondary voltage referred to Primary}$$

$$I'_2 = KI_2 = \text{Secondary current referred to Primary}$$

$$R'_2 = \frac{R_2}{K^2} = \text{Secondary resistance referred to Primary}$$



$$X'_{l2} = \frac{X_{l2}}{K^2} = \text{Secondary leakage Reactance referred to Primary.}$$

The iron losses or core losses of iron core

$$P_i = P_h + P_e$$

Where

$P_h \rightarrow$  Hysteresis loss

$P_e \rightarrow$  Eddy current loss

$$P_h = K_h B_m^{1.6} f \quad \& \quad P_e = K_e B_m^2 f^2$$

$B_m \rightarrow$  Peak flux density,

$f \rightarrow$  Frequency

Magnetising flux

$$\phi_m = \frac{1}{\sqrt{2}\pi N_1} \left( \frac{E_1}{f} \right)$$

$\Rightarrow$

$$B_m = \frac{1}{\sqrt{2}\pi N_1 A} \left( \frac{E_1}{f} \right)$$

Let

$$P_e \propto E_1^2 \quad (\text{approximated})$$

&

$$P_e \propto E_1^2$$

So

$$P_i \propto E_1^2$$

Hence


$$P_i = \frac{E_1^2}{R_i}$$

where

$R_i \rightarrow$  is constant

$R_i \rightarrow$  core loss resistor

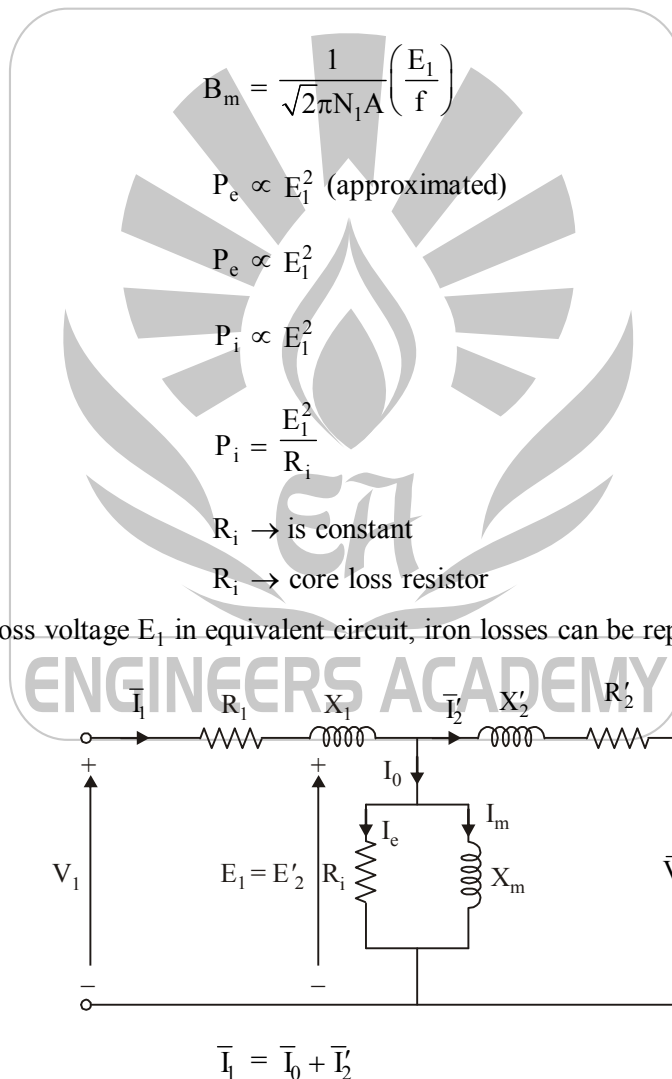By connecting  $R_i$  across voltage  $E_1$  in equivalent circuit, iron losses can be represented



Where no load current  $\bar{I}_0 = \bar{I}_e + \bar{I}_m$

$\bar{I}_0$  is approximately 4-5% of rated or full load current.

$$\bar{E}_1 = \bar{V}_1 - \bar{I}_1(R_1 + jX_1)$$


Let primary leakage impedance drop is neglected

$$E_1 \approx V_1 \text{ so no load current}$$

$$\bar{I}_0 = \frac{\bar{E}_1}{\bar{Z}_0} \approx \frac{\bar{V}_1}{\bar{Z}_0}$$

Where  $\bar{Z}_0$  is the impedance of magnetising branch

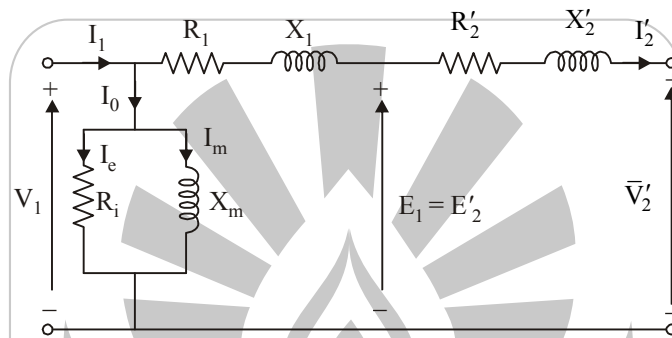Hence  $\bar{Z}_0$  can also be connected across  $\bar{V}_1$  so approximated equivalent circuit is





### 1.4 OPEN CIRCUIT AND SHORT CIRCUIT TEST

These test are performed to determine the circuit constants, efficiency and regulation without actually loading the Transformer.
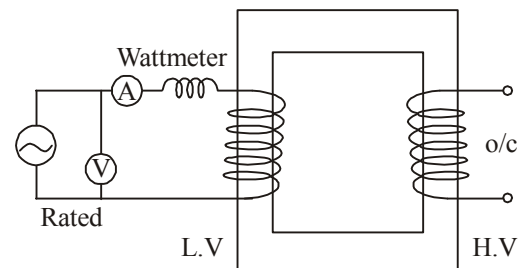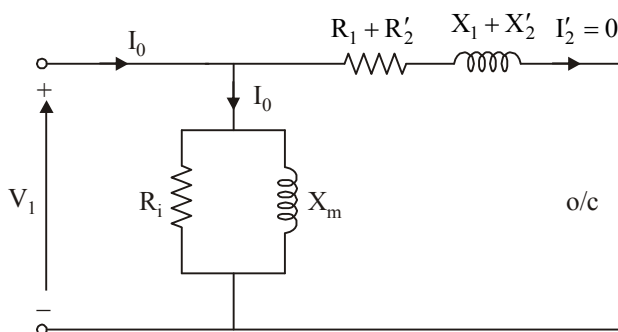
#### Open Circuit Test or No Load Test

To determine iron loss, As iron loss depends upon the applied voltage so it is performed at rated voltage hence it is performed on L.V side



**Readings**

$$V_0 \quad I_0 \quad P_i$$


Where  $V_0$  is the rated voltage applied.

$$P_i = \frac{V_0^2}{R_i}$$

$$\Rightarrow R_i = \frac{V_0^2}{P_i}$$

$$G_i = \frac{1}{R_i}$$
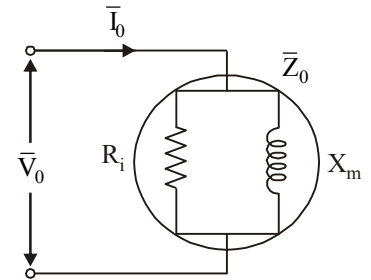
$$\frac{1}{Z_0} = \frac{1}{R_i} + \frac{1}{jX_m} = \frac{1}{R_i} - j\frac{1}{X_m}$$



$$\bar{Y}_0 = G_i - jB_m$$

$\bar{Y}_0$  admittance

$$|Y_0| = \sqrt{G_i^2 + B_m^2}$$

$$Z_0 = \frac{V_0}{I_0} \text{ and } Y = \frac{I_0}{V_0}$$


Susceptance

$$B_m = \sqrt{Y_0^2 - G_i^2}$$

Reactance

$$X_m = \frac{1}{B_m}$$

## 1.5 SHORT CIRCUIT TEST OR S.C. TEST

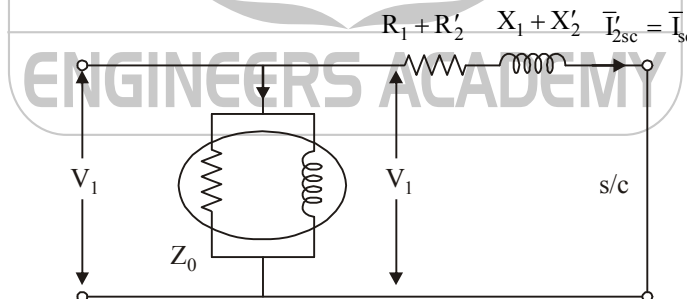


**Short** circuit test is performed to determine Cu-loss, As Cu-loss depends upon load current so short circuit test is performed at rated current.

To flow the rated current in short circuit condition reduced voltage upto 5% of rated voltage is required.

So short circuit test is performed at H.V side or low current side.

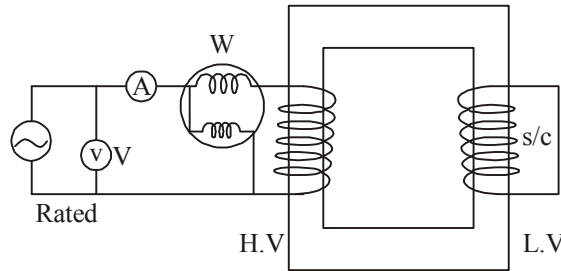
## Reduced Voltage is Applied for SC Test

At reduced voltage the no load current  $I_0$  will be very very small, so it can be neglected.



$$Z_{sc} = R + jX$$

$$Z_{sc} = \sqrt{R^2 + X^2}$$

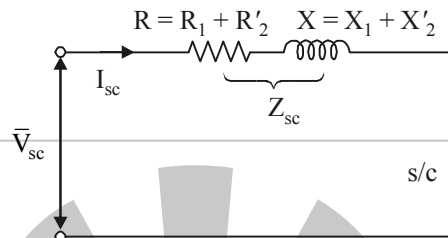

**Reading**

$$V_{sc} \quad I_{sc} \quad P_{sc}$$

rated value      Cu-loss

$$P_{sc} = I_{sc}^2 R \Rightarrow R = \frac{P_{sc}}{I_{sc}^2}$$

$$R = \frac{P_{sc}}{I_{sc}^2}$$

$$Z_{sc} = \frac{V_{sc}}{I_{sc}}$$

$$X = \sqrt{Z_{sc}^2 - R^2}$$

## 1.6 TRANSFORMER EFFICIENCY

The ratio of output power to the input power in a machine is known as the efficiency.

$$\eta = \frac{P_0}{P_{in}} = \frac{P_0}{P_0 + P_L}$$

Power input = Power output + Losses

$$P_{in} = P_0 + \text{Losses}$$

$$\% \eta = \frac{\text{Output}}{\text{Output} + \text{Losses}} \times 100$$

## Losses


### 1. Iron loss or core loss

This is constant with respect to load current

$$P_i = \frac{V_1^2}{R_i}$$
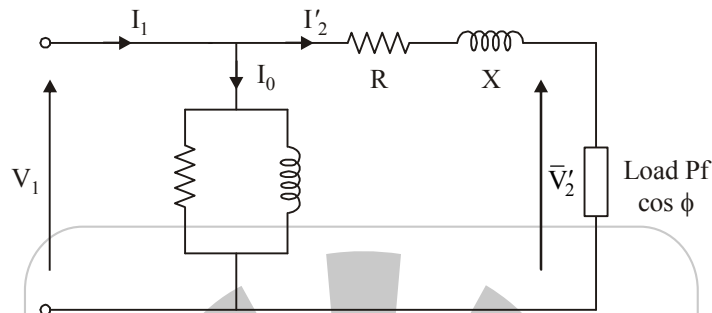
### 2. Cu loss or load loss

Varies with respect to load current  $I_2'^2 (R_1 + R_2')$



Power output

$$P_0 = V_2' I_2' \cos \phi$$

$$V_2' = \frac{V_2}{K}, \quad I_2' = K I_2, \quad K = \frac{N_2}{N_1}$$

$$P_0 = V_2' I_2' \cos \phi = \frac{V_2}{K} (K I_2) \cos \phi$$

At rated or full load current

So

$$= V_2 I_{2fl}$$

$x = 0.5 = 50\%$  of rated load or half full load

$$P_0 = V_2 I_2 \cos \phi$$

∴ At a load current

∴

$$I_2 = x I_{2fl}$$

$$P_0 = V_2 (x I_{2fl}) \cos \phi \quad x \leq 1$$

$$P_0 = x V_2 I_{2fl} \cos \phi$$

Load VA

$$S_L = V_2 I_2 = V_2 (x I_{2fl}) = x S_0$$

Where

$$[S_0 = V_2 I_{2fl}]$$

### 1. Iron Loss i.e. constant loss ( $P_i$ )